

## 21. HALF ADDER

**EXP.NO: 21**

**AIM:** To design and implement the two bit half adder using Logisim simulator.

### PROCEDURE:


- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the XOR gate and AND gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.

### TRUTH TABLE:


Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \text{ XOR } B \quad C = A \text{ AND } B$$


Logical Diagram:

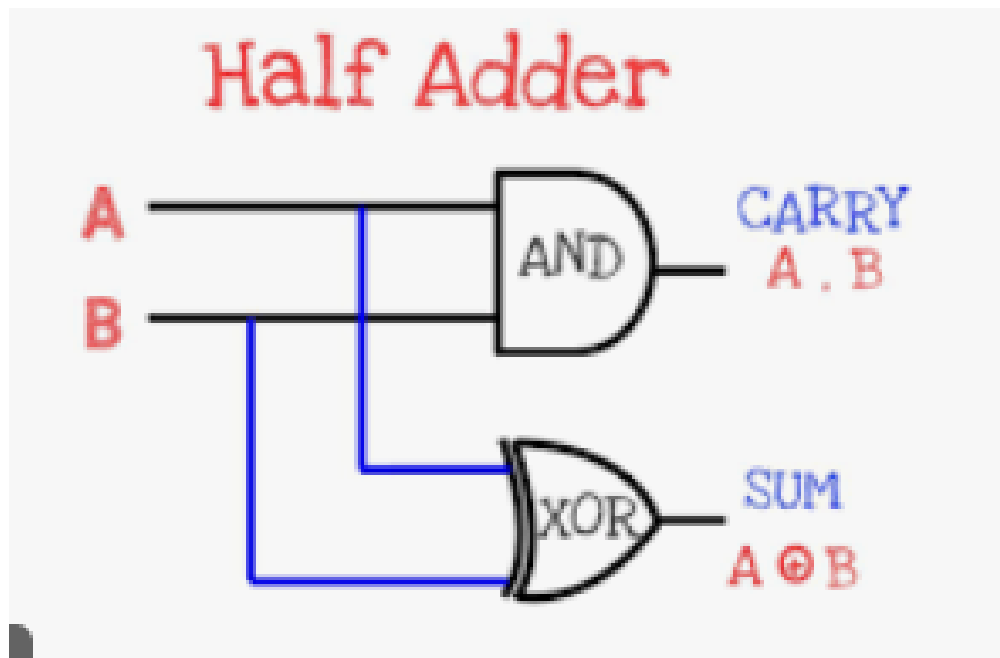

Half Adder using NAND Gates:

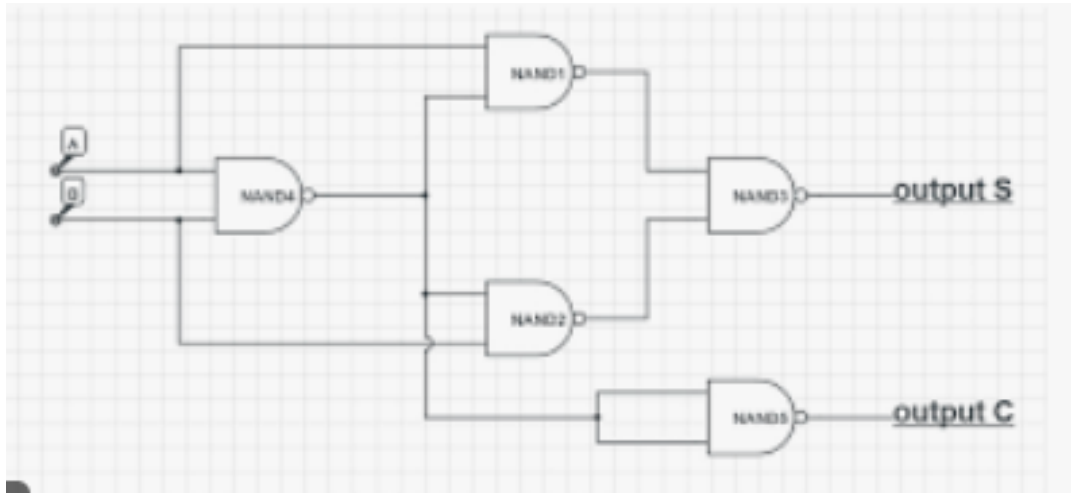

Half Adder using NOR Gates:

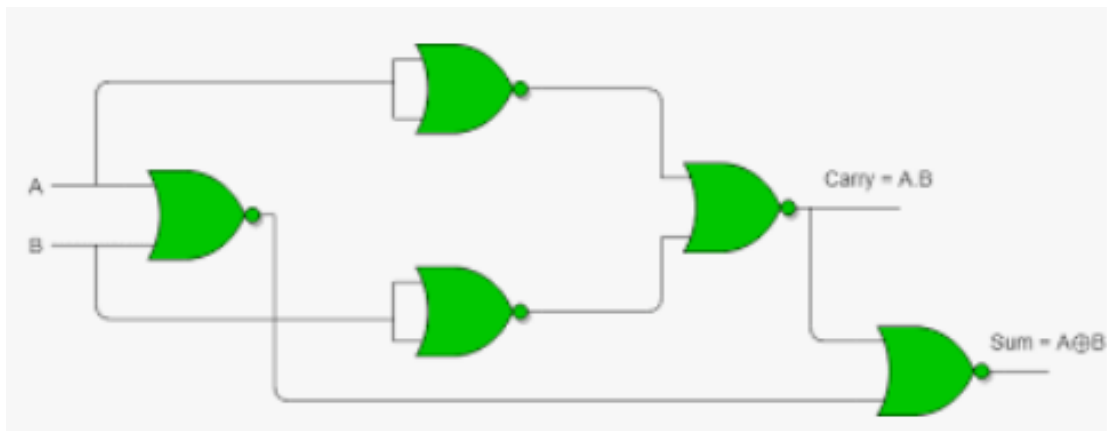

**OUTPUT**

**RESULT:** Thus 2-bit half adder has been designed and implemented successfully using logisim simulator.

## 22. TWO BIT HALF SUBTRACTOR

**EXP.NO: 22**

**AIM:** To design and implement the two bit half subtractor using Logisim simulator.

**PROCEDURE:**

- 1) Pick and place the necessary gates.
- 2) Insert 2 inputs into the canvas.
- 3) Connect the inputs to the OR gate, AND gate and NOT gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.


**TRUTH TABLE:**

A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


$\text{Diff} = A'B + AB'$

$\text{Borrow} = A'B$


Logical Diagram:

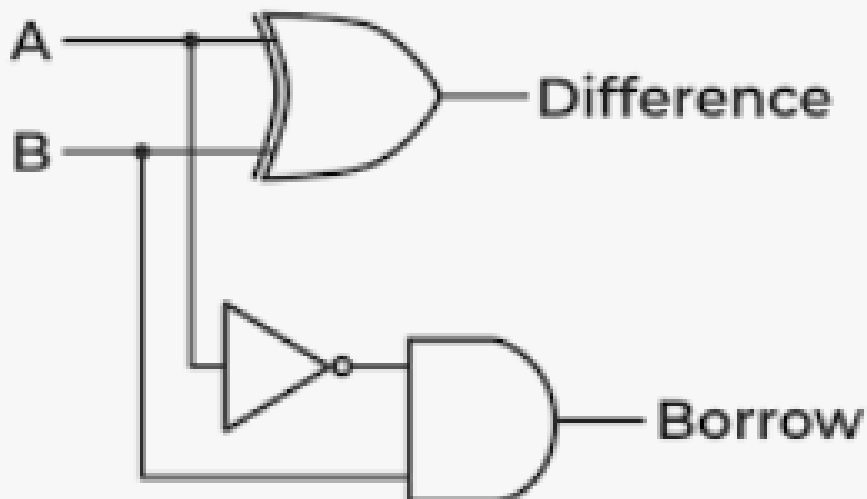

Half Subtractor using NAND Gates:

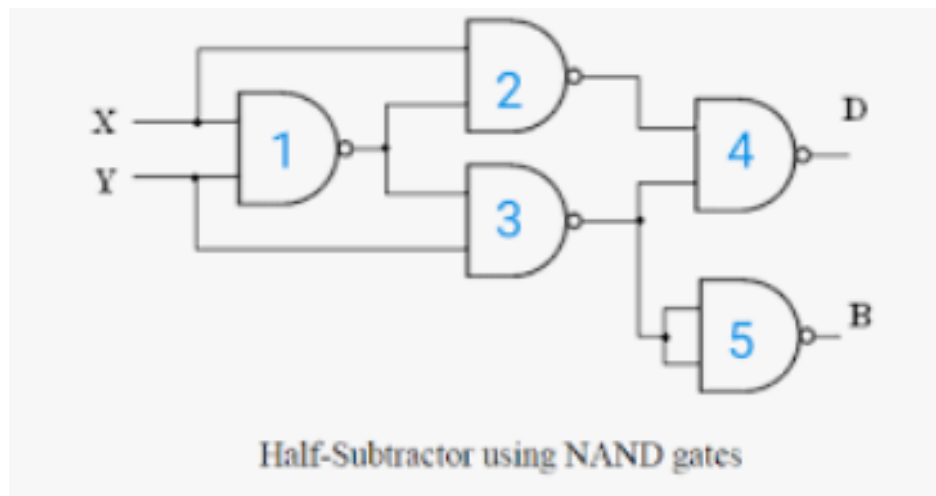

Half Subtractor using NOR Gates:

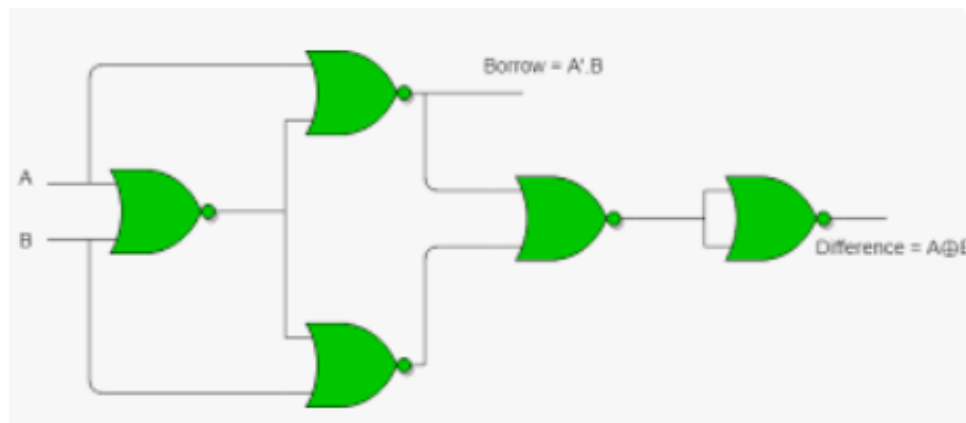

OUTPUT

**RESULT:** Thus 2-bit half subtractor has been designed and implemented successfully using logisim simulator.

### 23. FULL ADDER

**EXP.NO: 23**

**AIM:** To design and implement the full adder using Logisim simulator.

**PROCEDURE:**

- 1) Pick and place the necessary gates.
- 2) Insert 3 inputs into the canvas.
- 3) Connect the inputs to the XOR gate, AND gate and OR gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.


**TRUTH TABLE:**

Inputs			Outputs	
A	B	C <sub>in</sub>	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$\text{Sum} = (A \oplus B) \oplus C_{in}$$

$$\text{Carry} = A.B + (A \oplus B)$$


Logical Diagram:

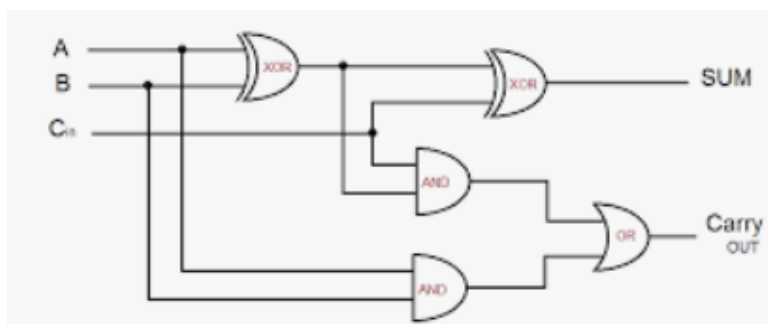

Full adder using NAND Gates:

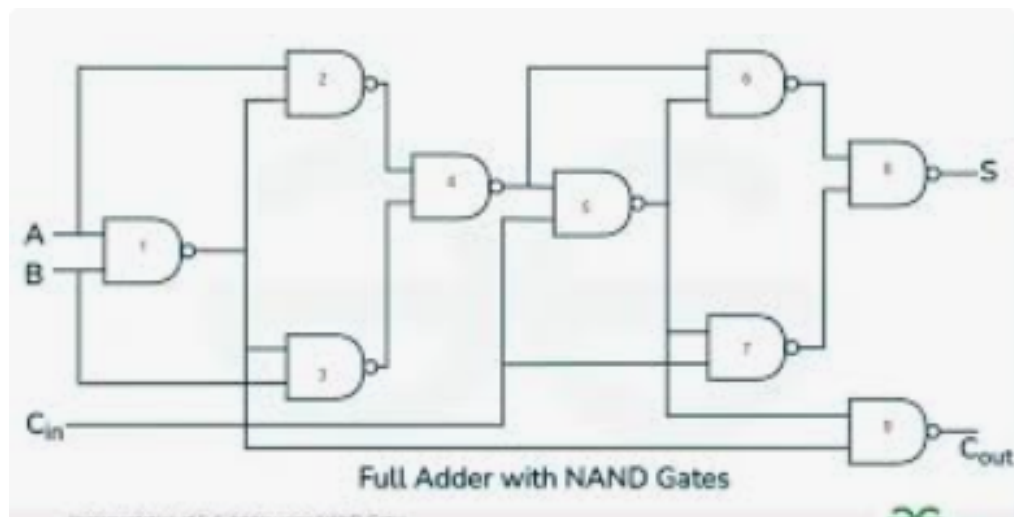

Full adder using NOR Gates:

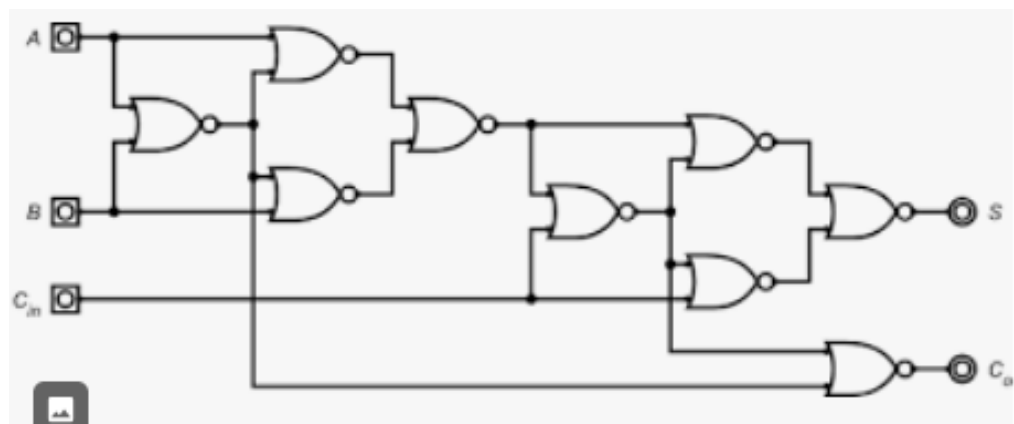

**OUTPUT**

**RESULT:** Thus full adder has been designed and implemented successfully using logisim simulator.

## 24. FULL SUBTRACTOR

**EXP.NO: 24**

**AIM:** To design and implement the full subtractor using Logisim simulator.

**PROCEDURE:**

- 1) Pick and place the necessary gates.
- 2) Insert 3 inputs into the canvas.
- 3) Connect the inputs to the XOR gate, AND gate and OR gate.
- 4) Insert 2 outputs into the canvas.
- 5) Make the connections using the connecting wires.
- 6) Verify the truth table.


**TRUTH TABLE:**

INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


$$\text{Diff} = (A \oplus B) \oplus \text{'Borrowin'}$$

$$\text{Borrow} = A'.B + (A \oplus B)'$$


Logic Diagram:

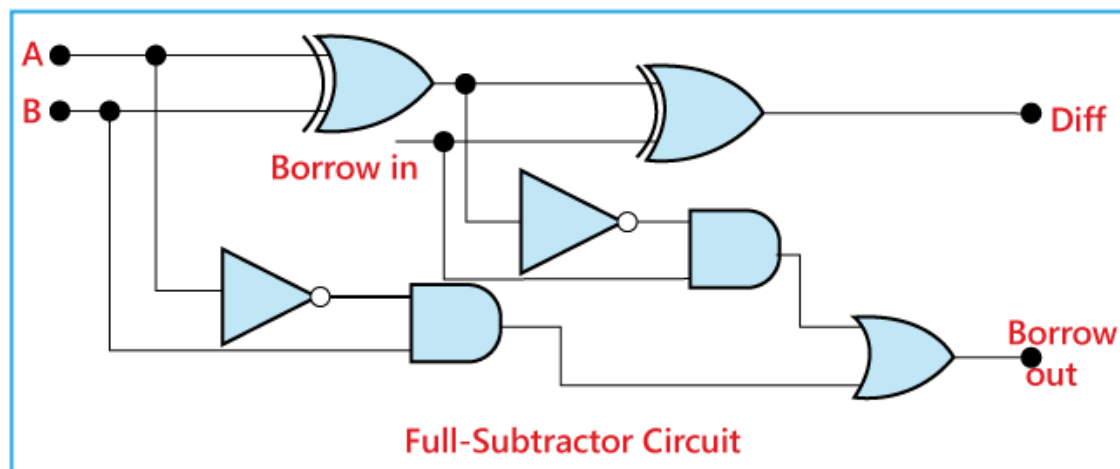

Full Subtractor using NAND Gates:

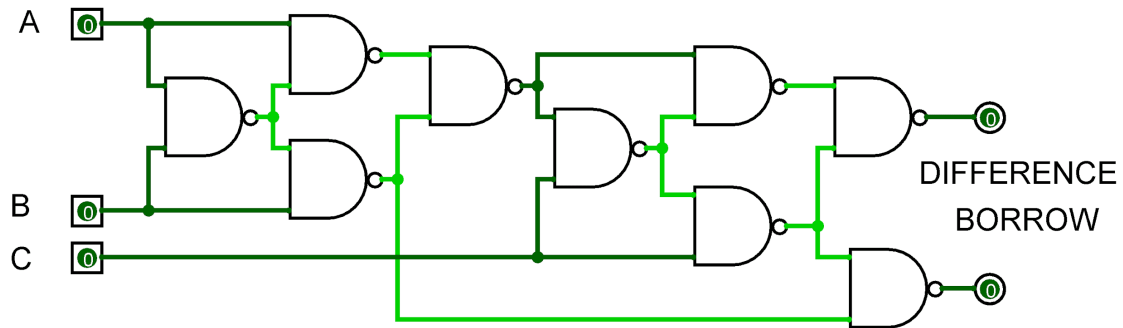

Full Subtractor using NOR Gates:

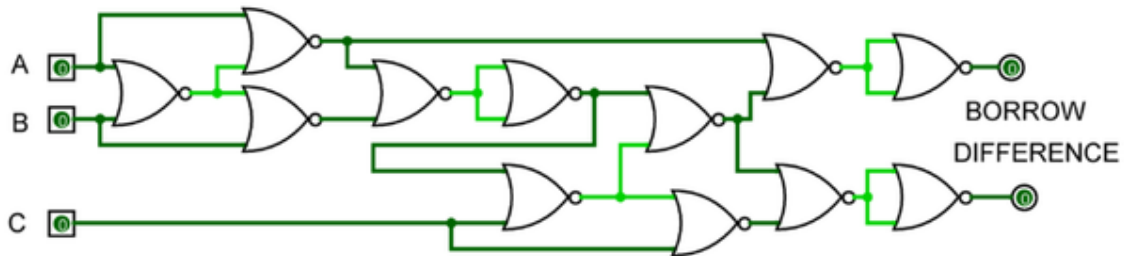

OUTPUT

**RESULT:** Thus full subtractor has been designed and implemented successfully using logisim simulator.